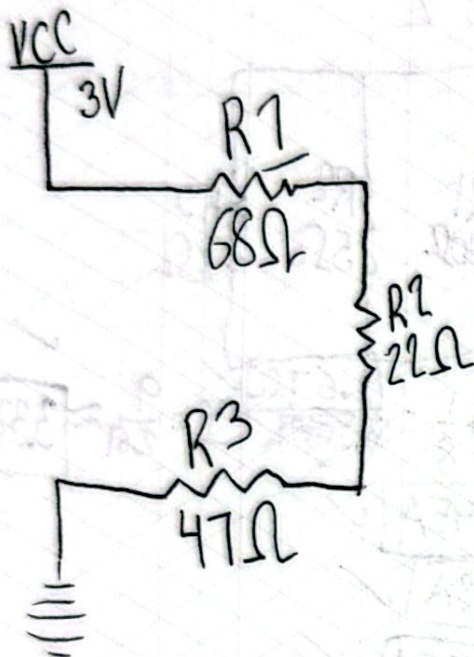





Pos.	Voltage	Current	Resistance
1	1.36	0.02	68
2	0.44	0.02	22
3	0.94	0.02	47
total	3	0.02	137

$$R_T = 68 + 22 + 47 = 137 \quad I = \frac{V_T}{R_T} = \frac{3}{137} = 0.02$$

$$R_1 = .02(68) = 1.36 \quad R_2 = .02(22) = .44 \quad R_3 = .02(47) = .94$$

~~$$V_T = 2.74$$~~

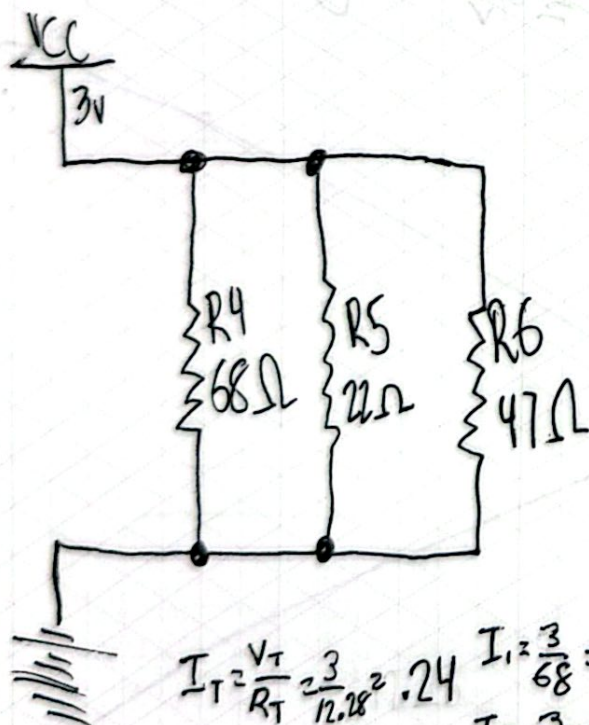

Pos.	Voltage	Current	Resistance
4	3	0.04	68
5	3	0.14	22
6	3	0.06	47
total	3	0.24	12.28

$$I_T = \frac{V_T}{R_T} = \frac{3}{12.28} = .24 \quad I_1 = \frac{3}{68} = .04$$

$$I_2 = \frac{3}{22} = .14 \quad I_3 = \frac{3}{47} = .06$$

$$R_T = \frac{1}{\left(\frac{1}{68}\right) + \left(\frac{1}{22}\right) + \left(\frac{1}{47}\right)} = 12.279$$

Signature: Jeremy C.Date: 09/03

Team Members:

Witness: Erik A.Date: 9/3N/AContinued From Page # N/AContinued On Page # N/A